



Fermilab





*Design
of an
Accelerator RF System*

Ralph J. Pasquinelli


Ralph J. Pasquinelli

Basic 1.5 eV accelerator

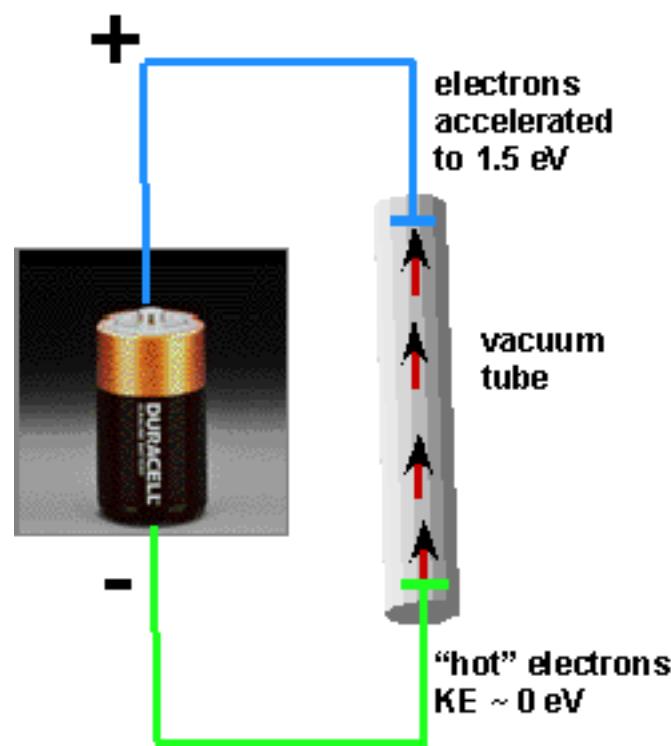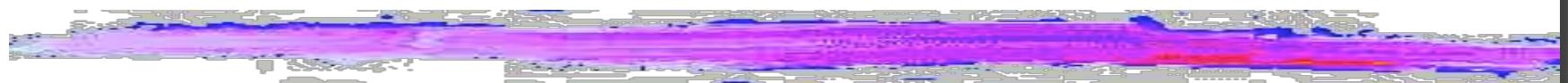

Ralph J. Pasquinelli

Basic Principle of Acceleration

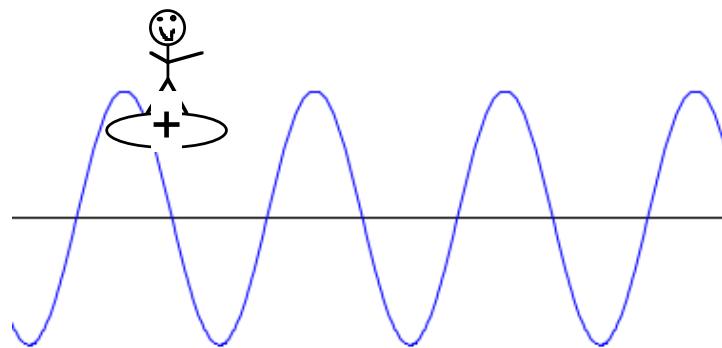


Ralph J. Pasquinelli

Building Blocks of a RF System





Ralph J. Pasquinelli

RF Cavity transformed from a LC circuit

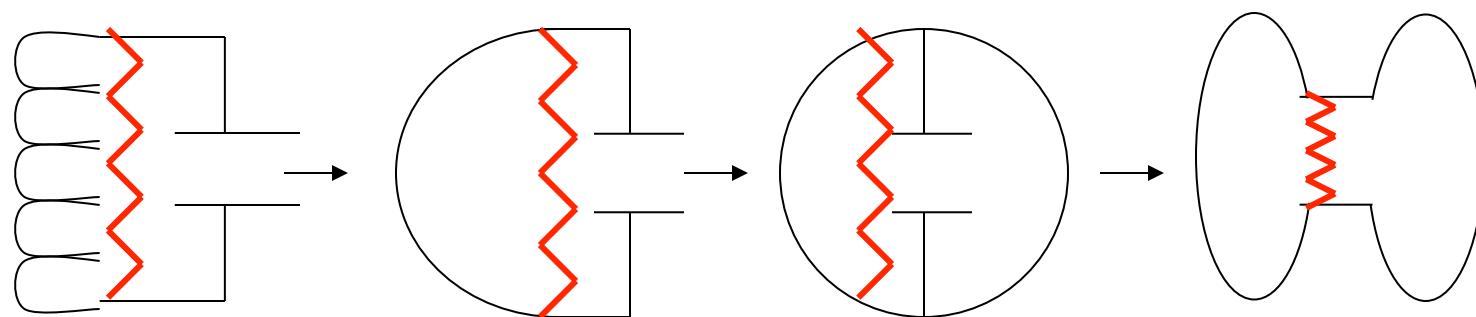

$$w_o = 2\pi f_o = \sqrt{\frac{1}{LC}}$$

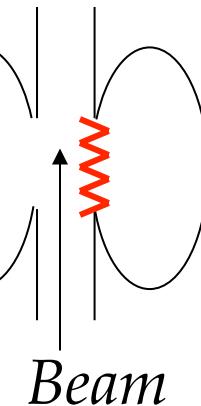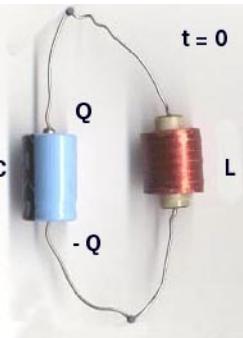

*Shunt
Impedance*

Ralph J. Pasquinelli


Cavity Q or Quality Factor



$Q = \text{Energy Stored}/\text{Energy Lost (per cycle)}$


$Q = f_o/\text{BW}$ (Center Frequency/Band Width)

$-3 \text{ dB} \pm 45 \text{ degrees}$

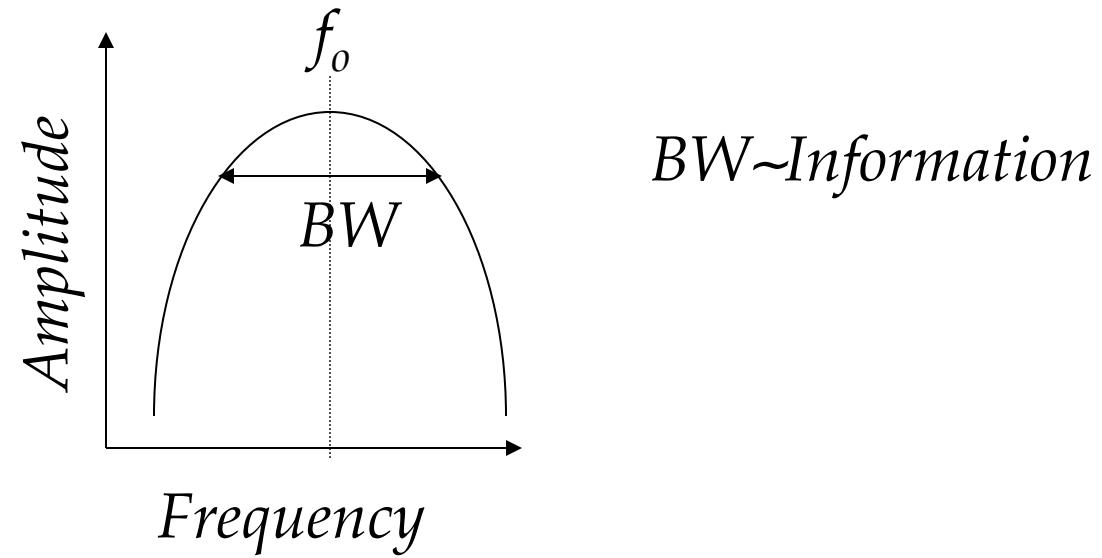

Ralph J. Pasquinelli

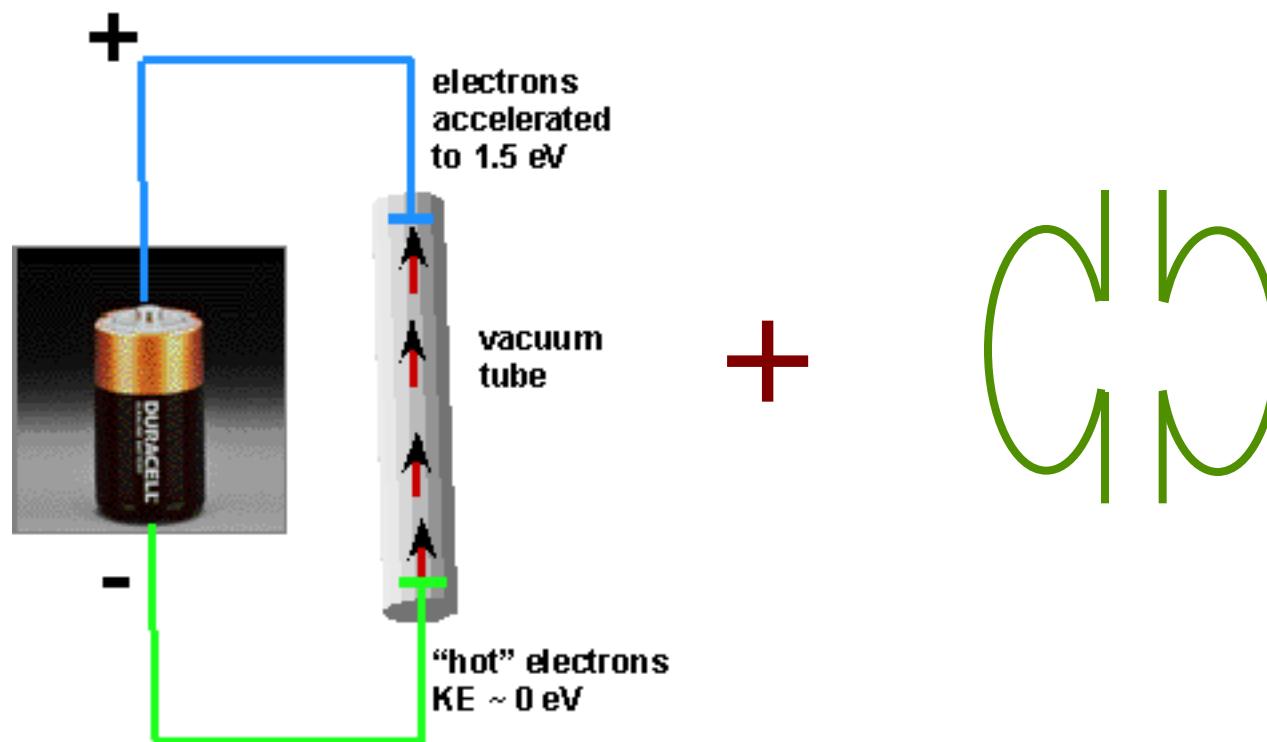Klystrons, IOT, Solid State Provides the RF Power



Ralph J. Pasquinelli

Invention of the Klystron

*Varian Brothers
Russell and Sigurd
Develop Klystron
In 1939 at Stanford*





*Named Klystron after
Greek verb klyzo which
expresses the breaking of
waves on the beach*

Ralph J. Pasquinelli



Klystron Operation

Electron Beam Velocity Modulation

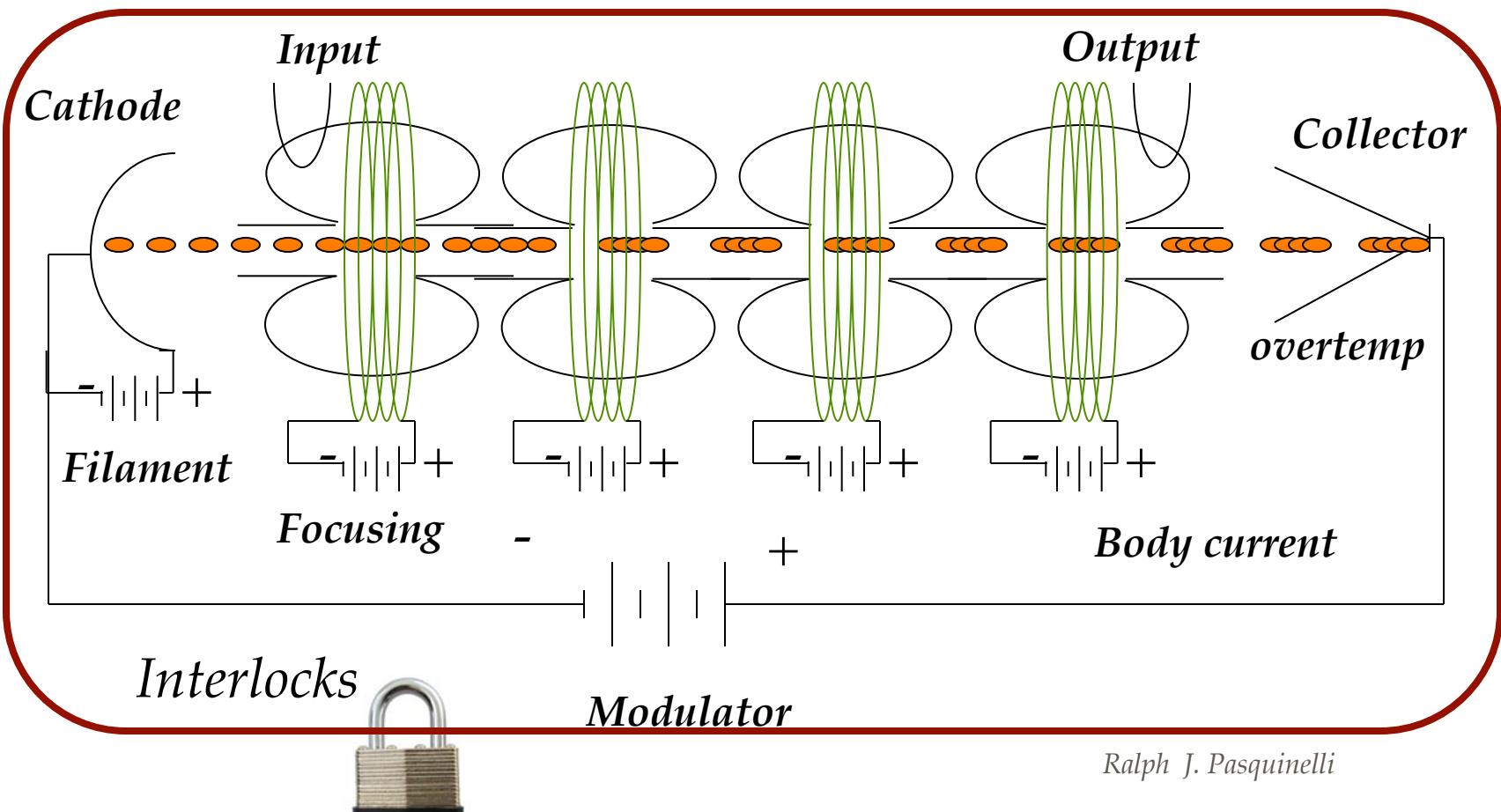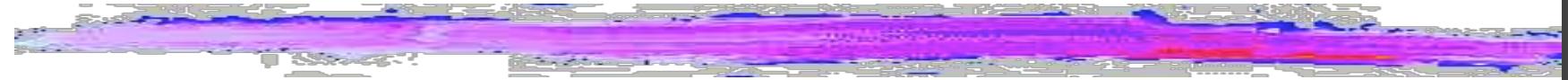

Ralph J. Pasquinelli

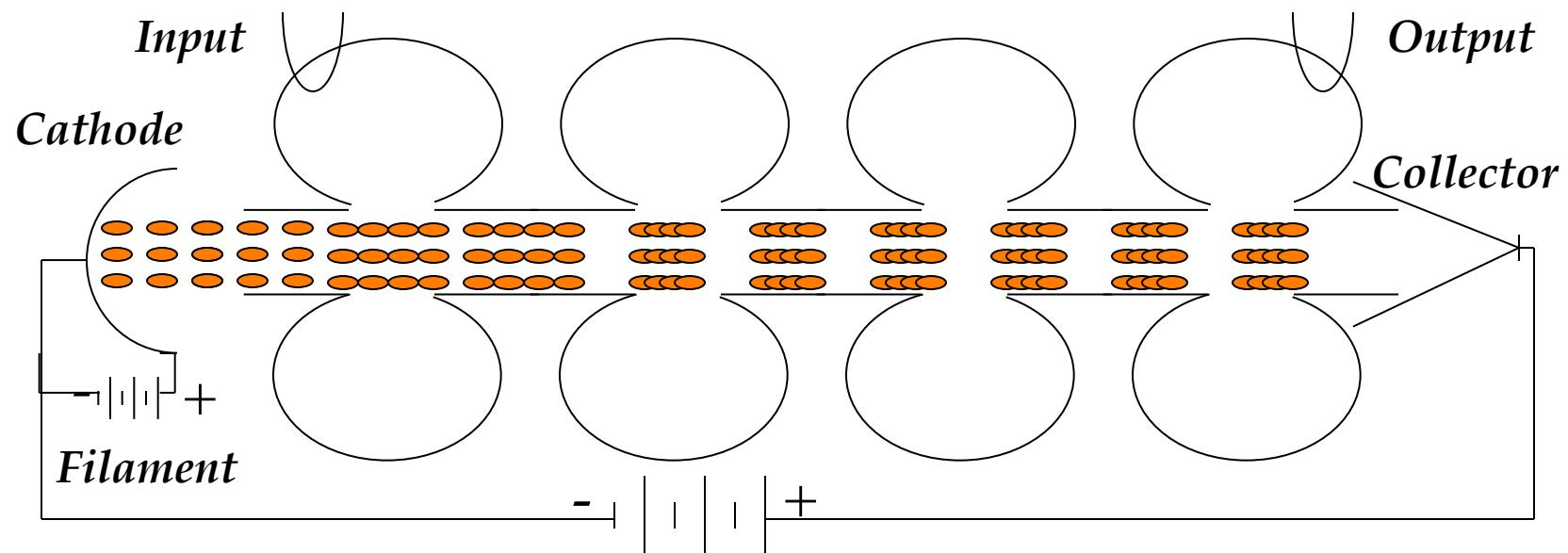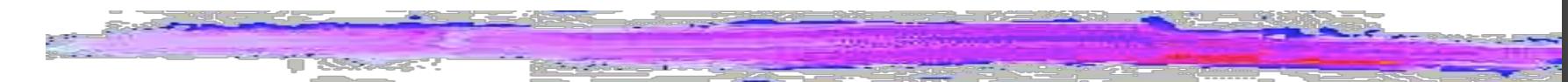Multi-Beam Klystron Operation Power Conversion Efficiency & Reduced Space Charge



Power = Electron Current x Cathode Voltage
Megawatts 10's of Amps 50-120 of Kilovolt

Modulator

Ralph J. Pasquinelli

Typical Klystron Parameters




<i>Power Gain</i>	$40\text{-}60 \text{ dB}$ ($10^4\text{-}10^6$)
<i>Power</i>	10^3 to 10^7 Watts
<i>Duty Cycle</i>	Continuous or Pulsed
<i>Frequency</i>	Hundreds MHz to Tens GHz
<i>Bandwidth</i>	1%
<i>Efficiency</i>	50%
<i>Cathode volts</i>	10's to 100's of kilovolts
<i>Klystron Life</i>	10,000-100,000 hours

Ralph J. Pasquinelli


Klystron Characteristics



10/25/91

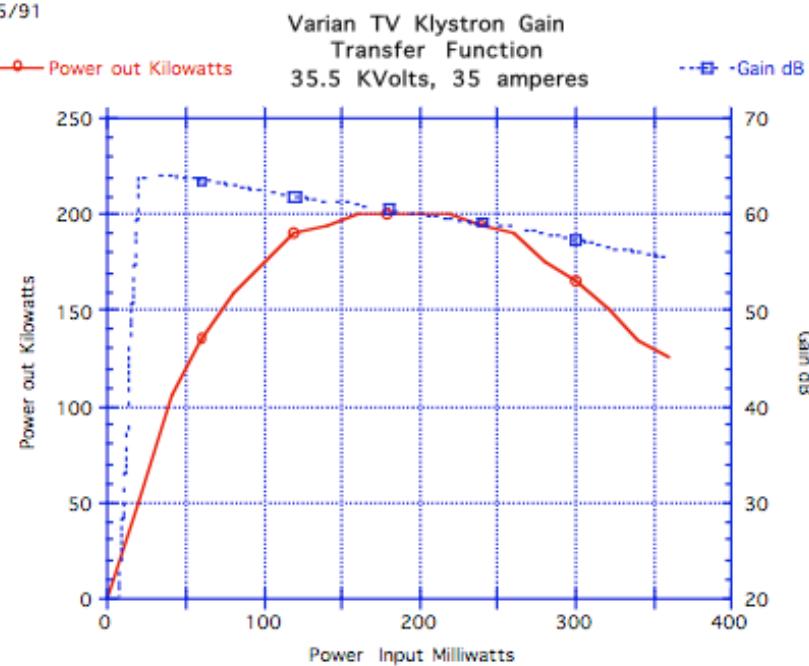

7/26/91

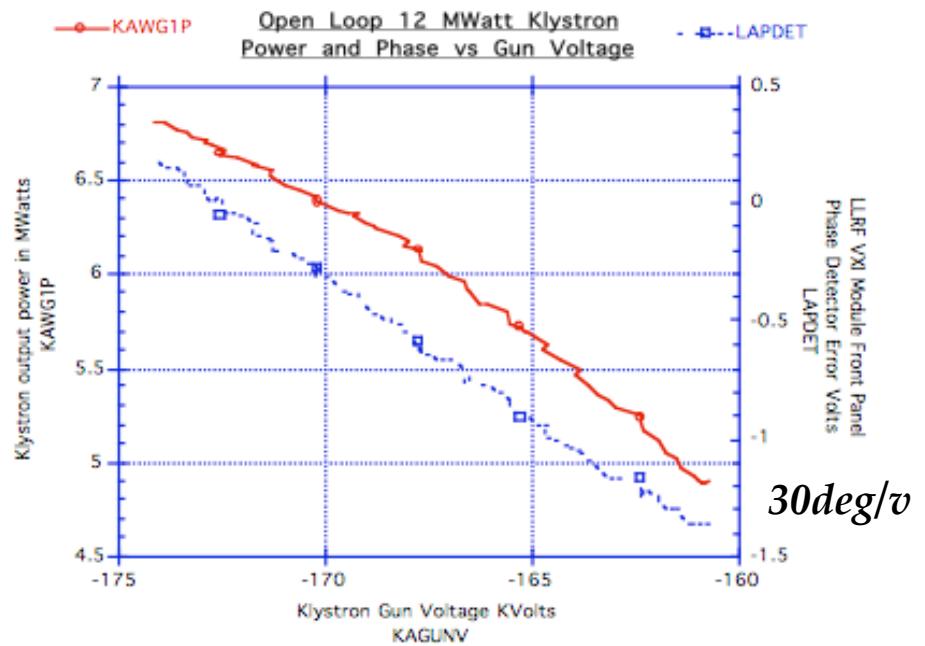


Power Gain Curve

Gain/Phase vs Gun Volts

Ralph J. Pasquinelli

Klystron Photos

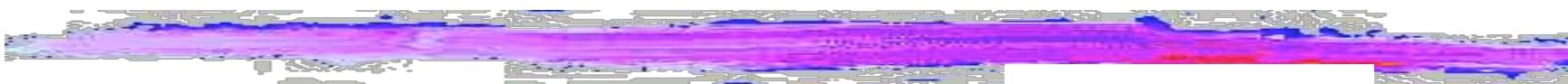

CPI VLK8301



Toshiba



TH 1801
Multi-Beam Klystron

10 MW peak - 150 kW av.
at 1.3 GHz




THALES

Ralph J. Pasquinelli

Inductive Output Tube (IOT) Operation

Electron Beam Grid Gated

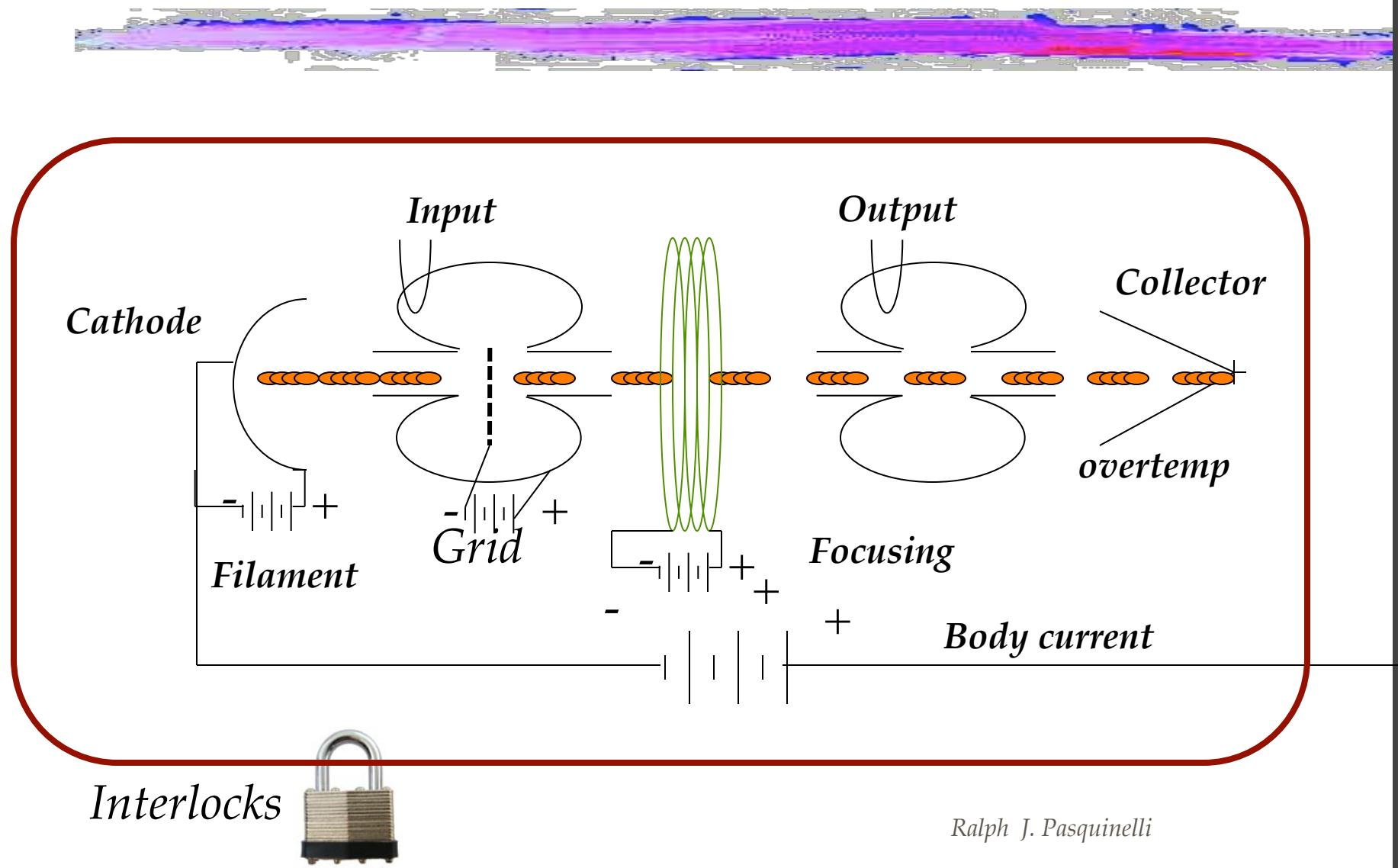


Typical IOT Parameters



<i>Power Gain</i>	<i>20-25 dB</i>
<i>Power</i>	<i>10^4 to 10^5 Watts</i>
<i>Duty Cycle</i>	<i>Continuous or Pulsed</i>
<i>Frequency</i>	<i>Hundreds MHz (UHF)</i>
<i>Bandwidth</i>	<i>1%</i>
<i>Efficiency</i>	<i>60-65%</i>
<i>Cathode volts</i>	<i>10's of kilovolts</i>
<i>IOT Life</i>	<i>10,000-50,000 hours</i>

Ralph J. Pasquinelli

IOT Characteristics

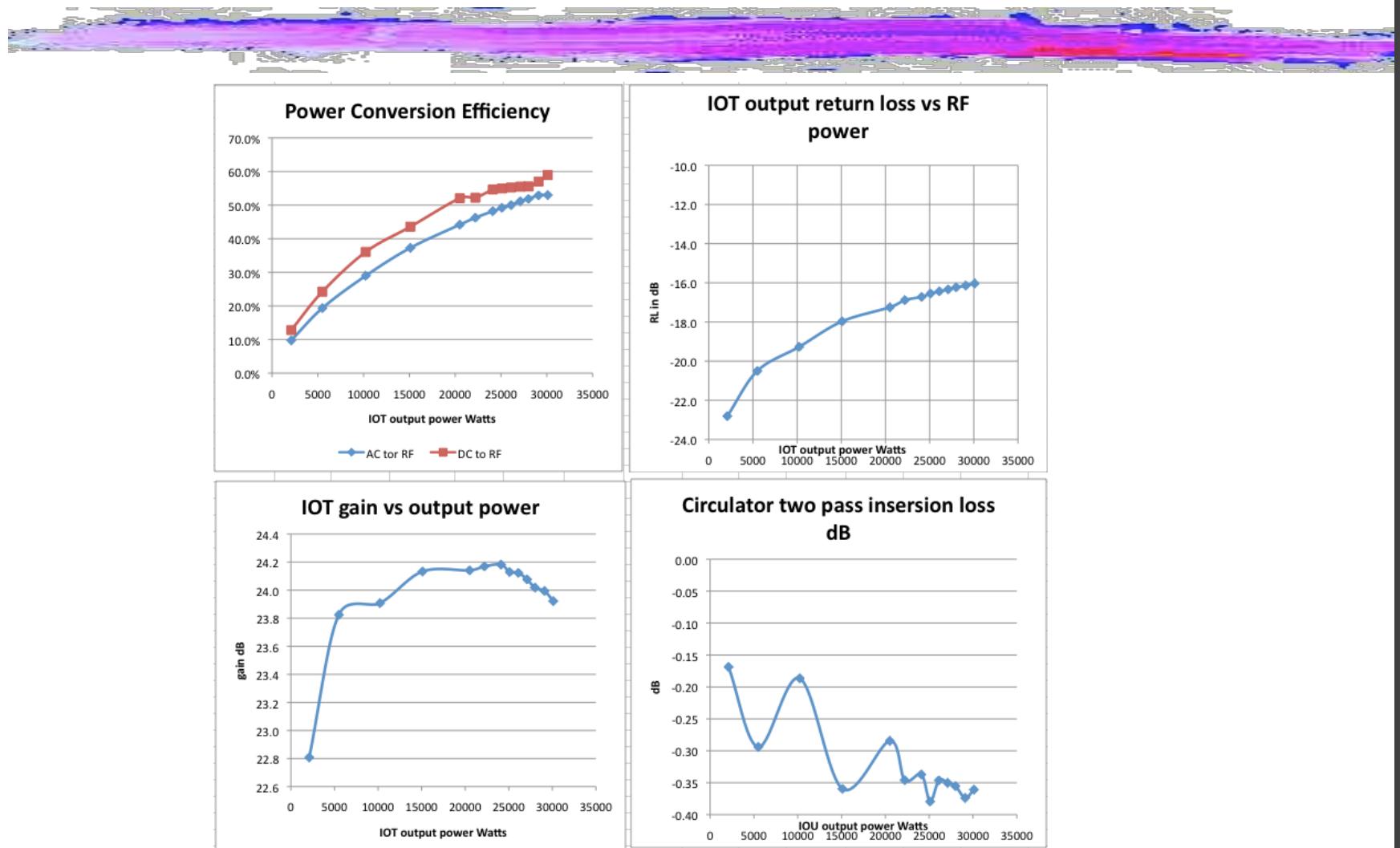


Ralph J. Pasquinelli

IOT Photos



Ralph J. Pasquinelli

Solid-State Topology

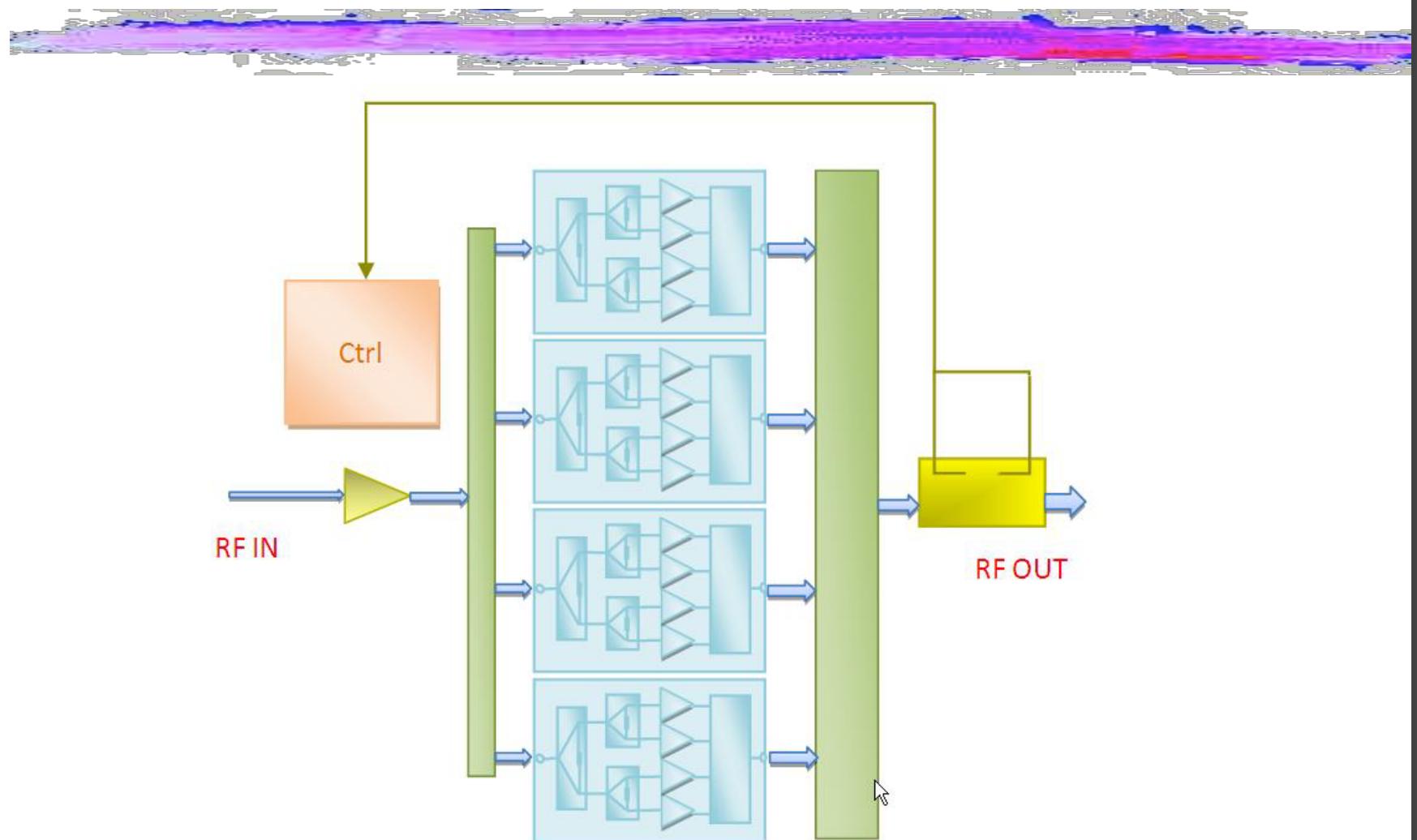

Ralph J. Pasquinelli


Typical Solid-state Parameters



<i>Power Gain</i>	$20\text{-}70 \text{ dB}$ ($10^2\text{-}10^7$)
<i>Power</i>	10^3 to 10^5 Watts
<i>Duty Cycle</i>	Continuous or Pulsed
<i>Frequency</i>	1 MHz to 2 GHz
<i>Bandwidth</i>	few % to decades
<i>Efficiency</i>	10-50%
<i>Voltage</i>	20-50 volts DC
<i>Life time</i>	10,000-200,000 hours

Ralph J. Pasquinelli

Typical Amplifier Module

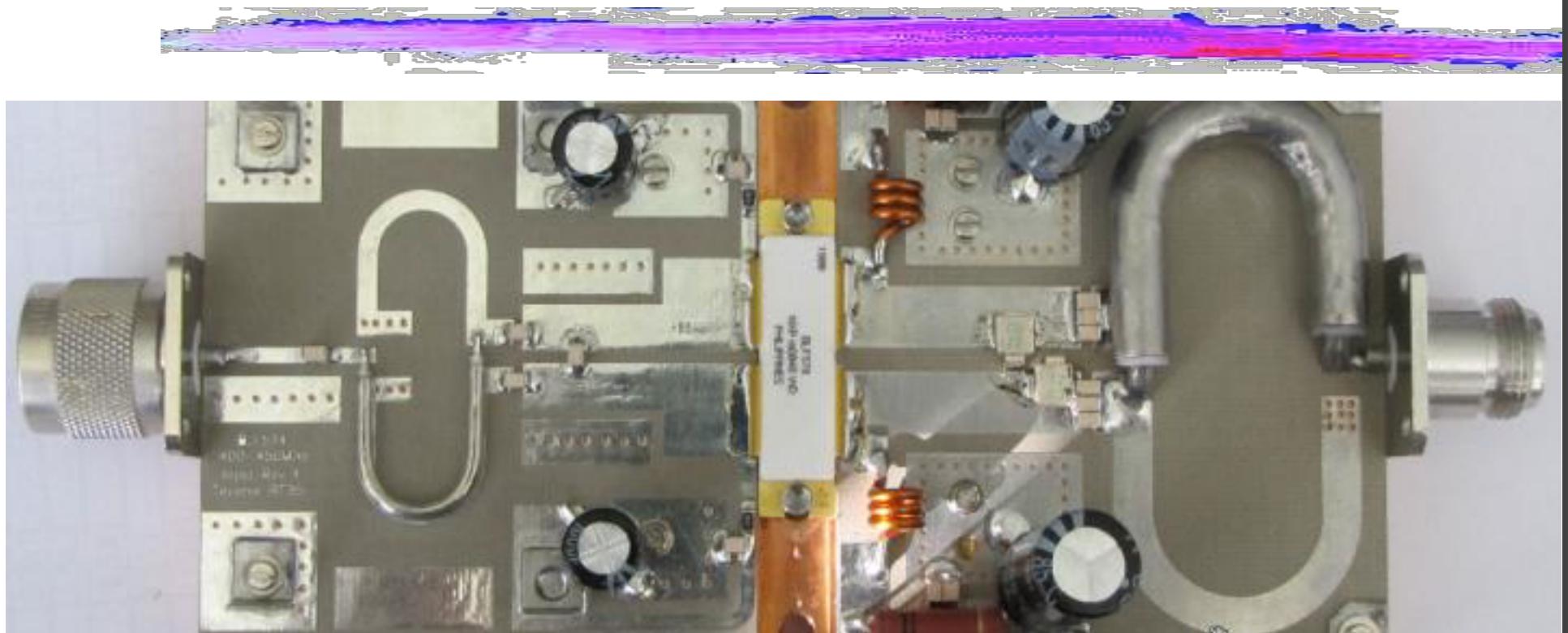


Ralph J. Pasquinelli

Bruker Solid-state 10 KW Amplifier



Ralph J. Pasquinelli

Power Transmission


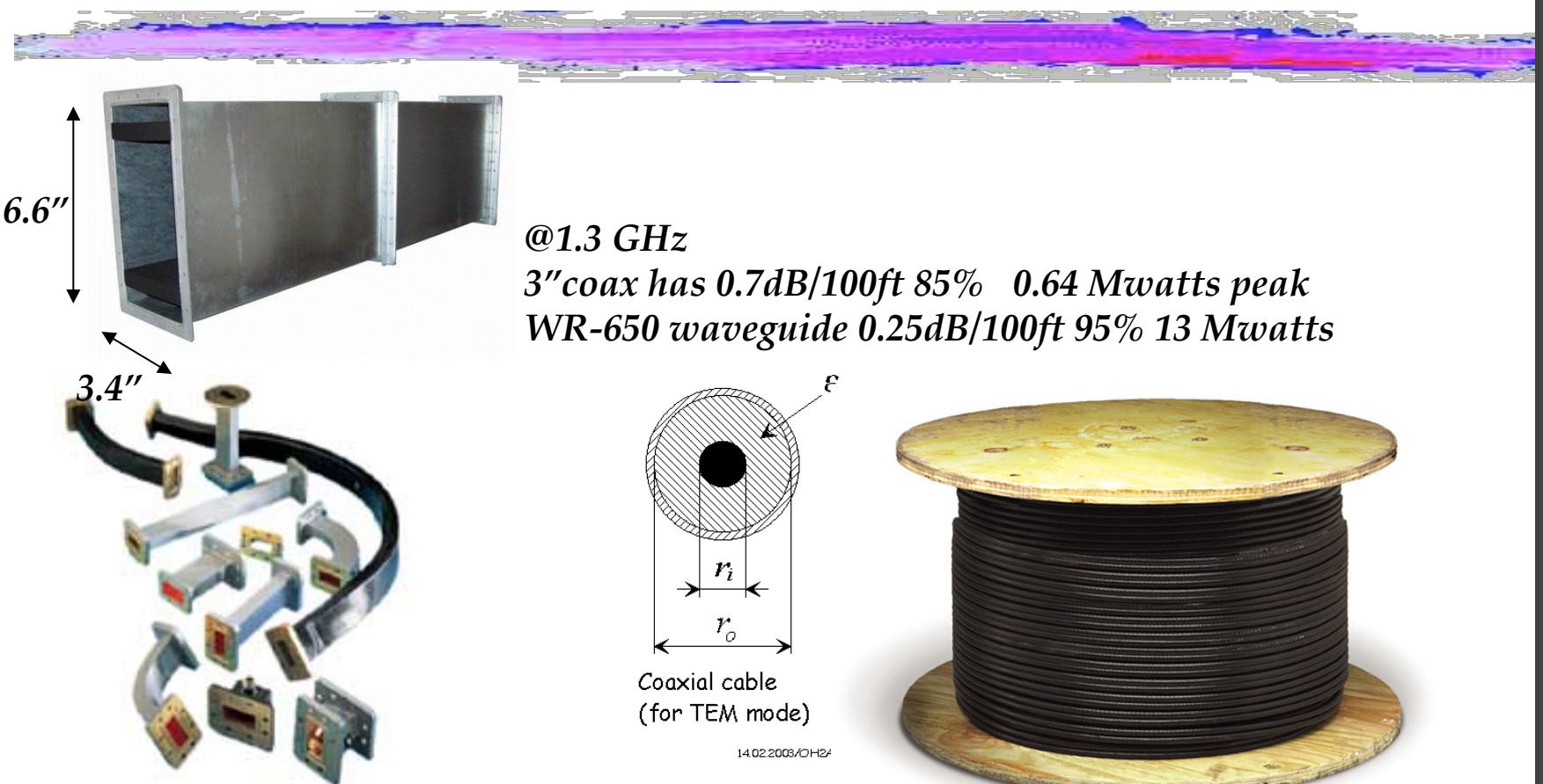


Waveguide

Coaxial Cable

Ralph J. Pasquinelli

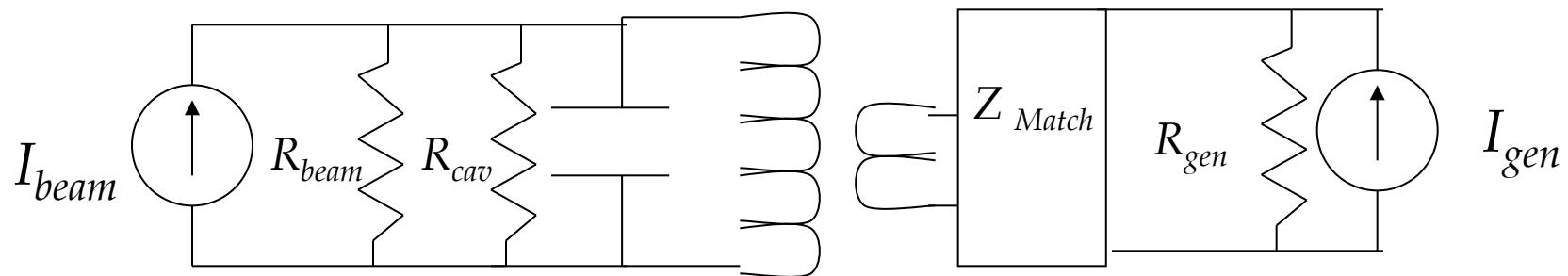
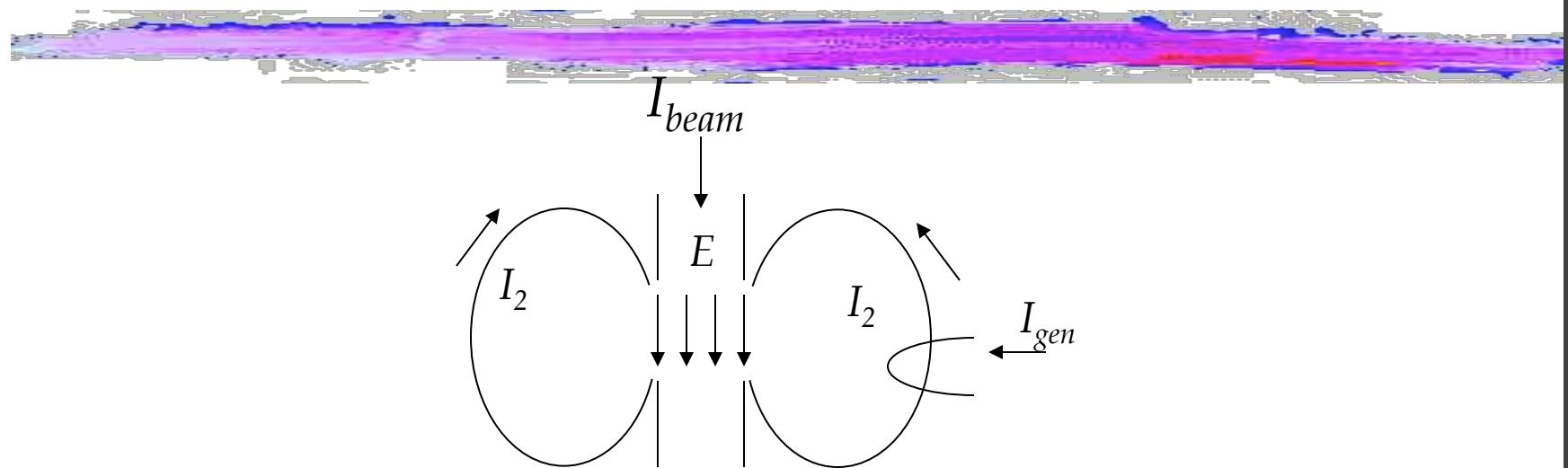
*To inject or extract energy
A coupling loop is used.*



*Equivalent
Circuit model*

Ralph J. Pasquinelli


Importance of Matching

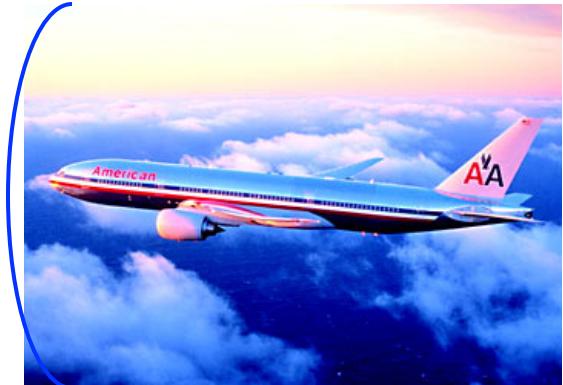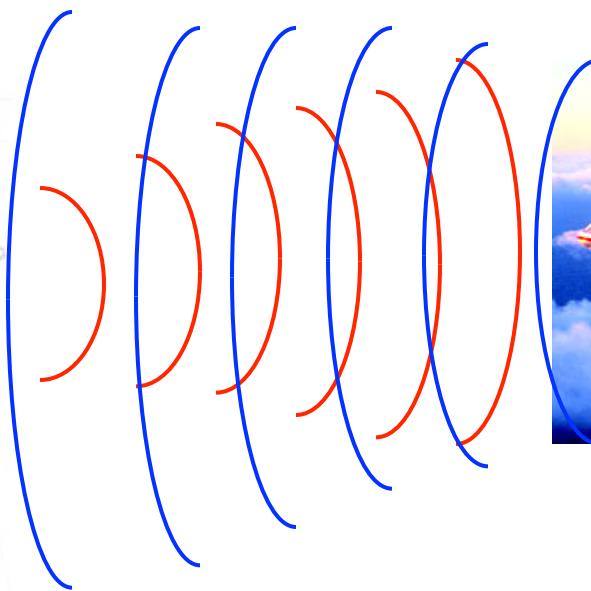

Radar works due to poor matching

Ralph J. Pasquinelli


Importance of Matching

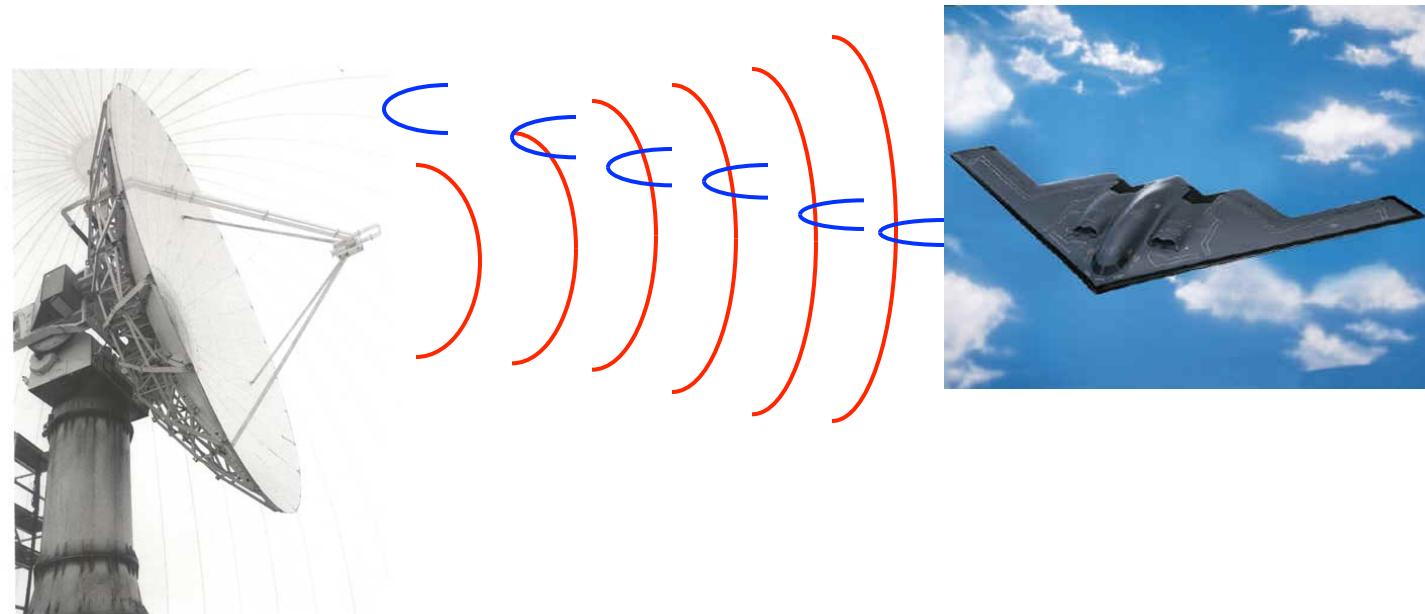

Better matching with the B2 harder to detect!

Ralph J. Pasquinelli

Microwave Matching Gizmos

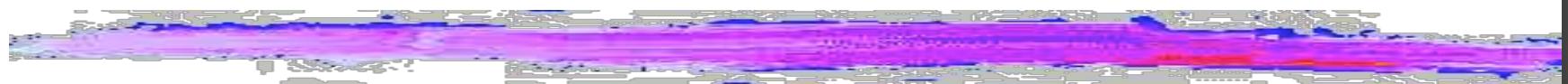

Directional Coupler



Three Stub Tuners



Circulator/Isolator





Waveguide Load

Ralph J. Pasquinelli

Cavity Model




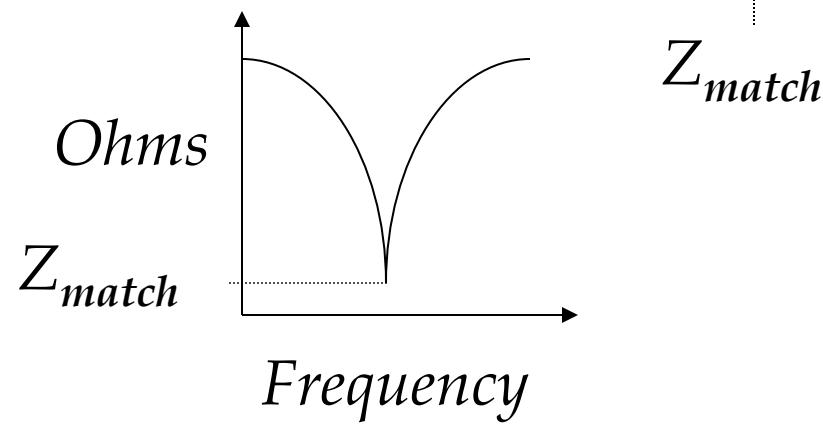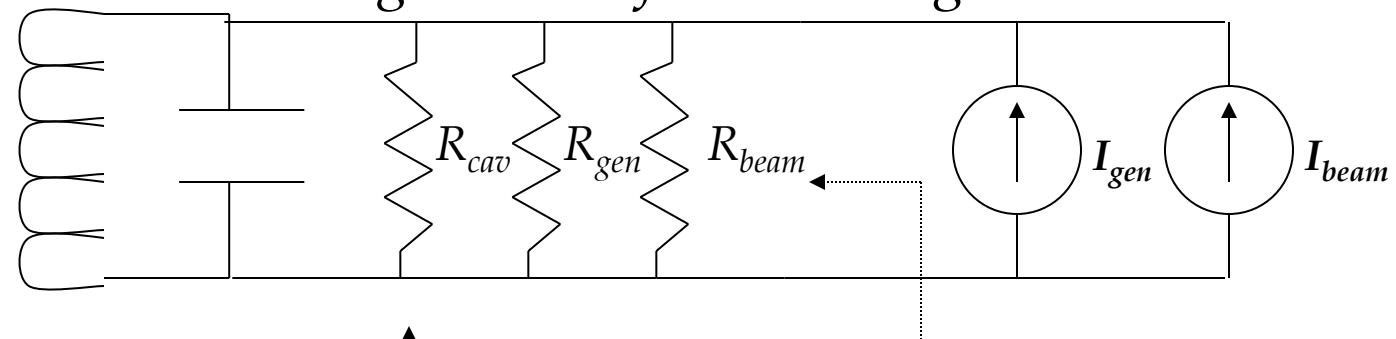*Further circuit simplification
and
assign values for modeling*



Ralph J. Pasquinelli

Design of a RF System

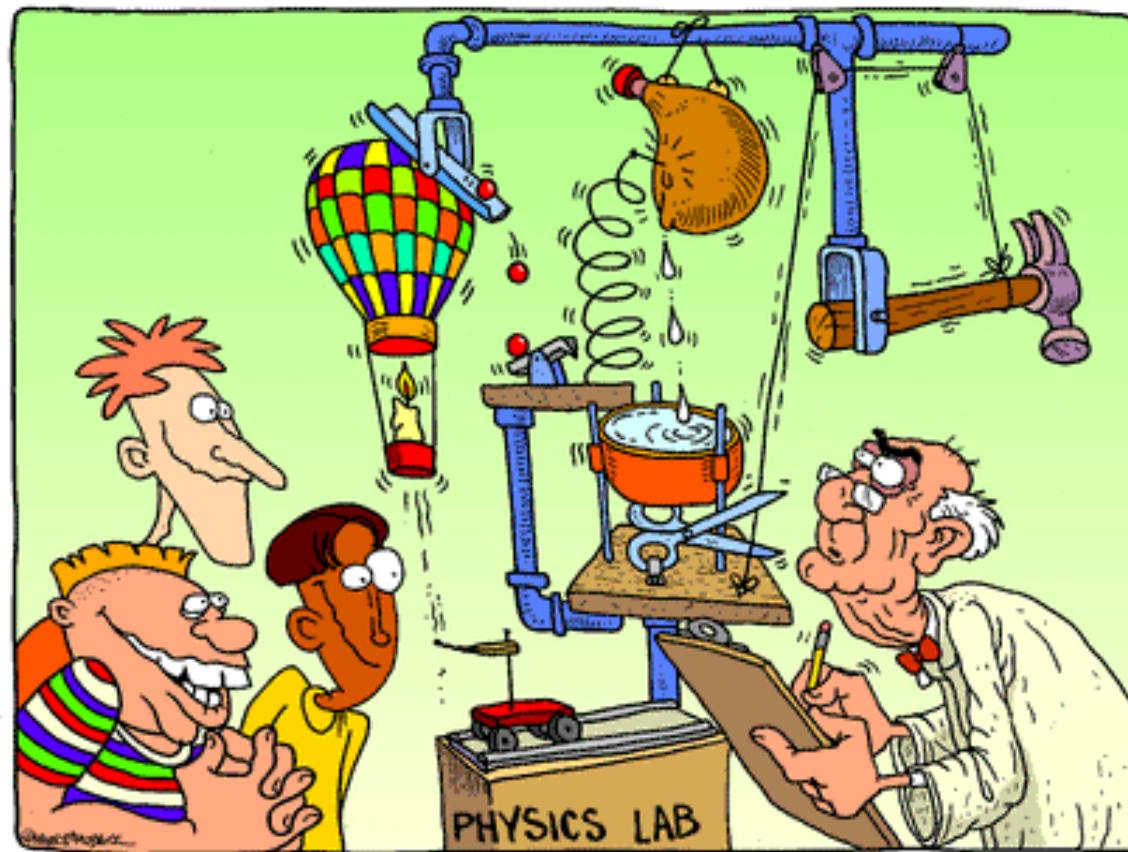

Ralph J. Pasquinelli

Questions to Ask



Duty Cycle?

Gradient possible?

Power source available?



TH 1801
Multi-Beam Klystron

10 MW peak - 150 kW av.
at 1.3 GHz

THALES

Ralph J. Pasquinelli


Need to Choose Frequency of Operation



Size Limitation?



Goldie Locks "just right!"

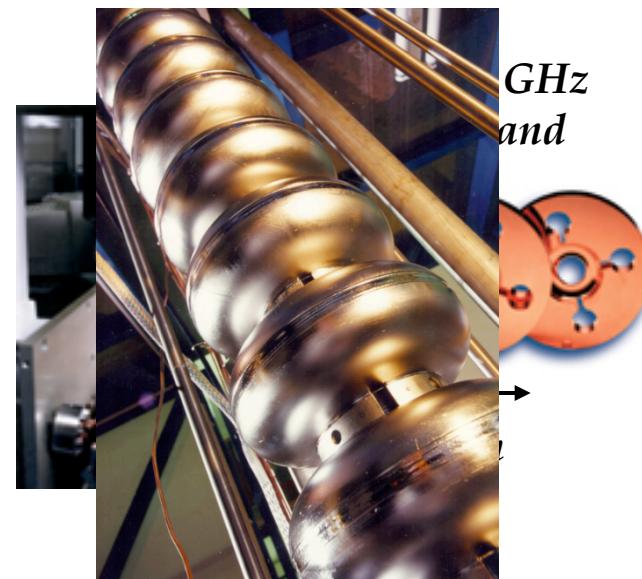

1.3 GHz Rf Shallow Cavity 70mm iris

Ralph J. Pasquinelli

Issues with Superconducting RF (SRF):







Narrow bandwidth due to high Q of 10^9

Pulsed RF fields exert mechanical detuning forces

Microphonic sensitivity

Ralph J. Pasquinelli

Lorentz Force Detuning

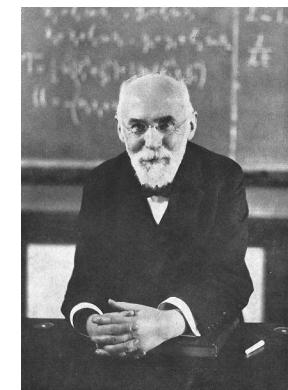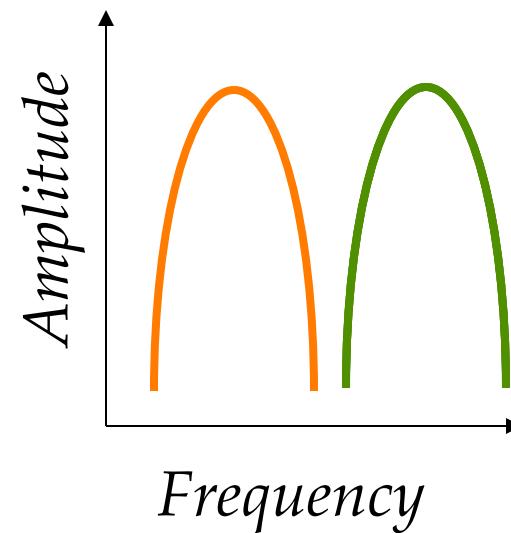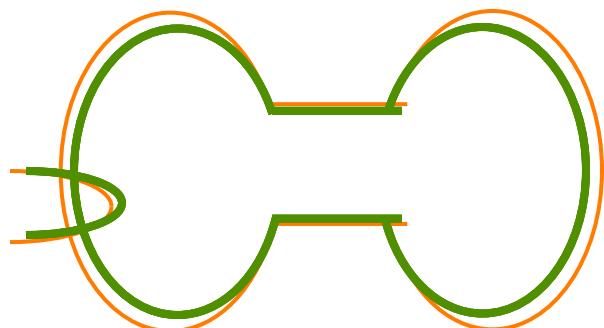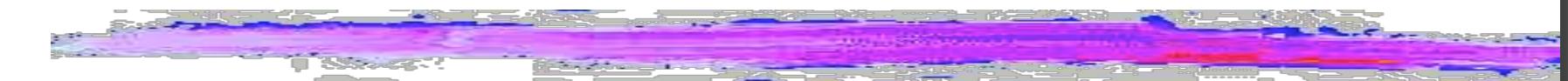


Ralph J. Pasquinelli

Dynamic Resonance Control



Piezoelectric tuner

M. Liepe, S. Simrock, W.D.-Moeller

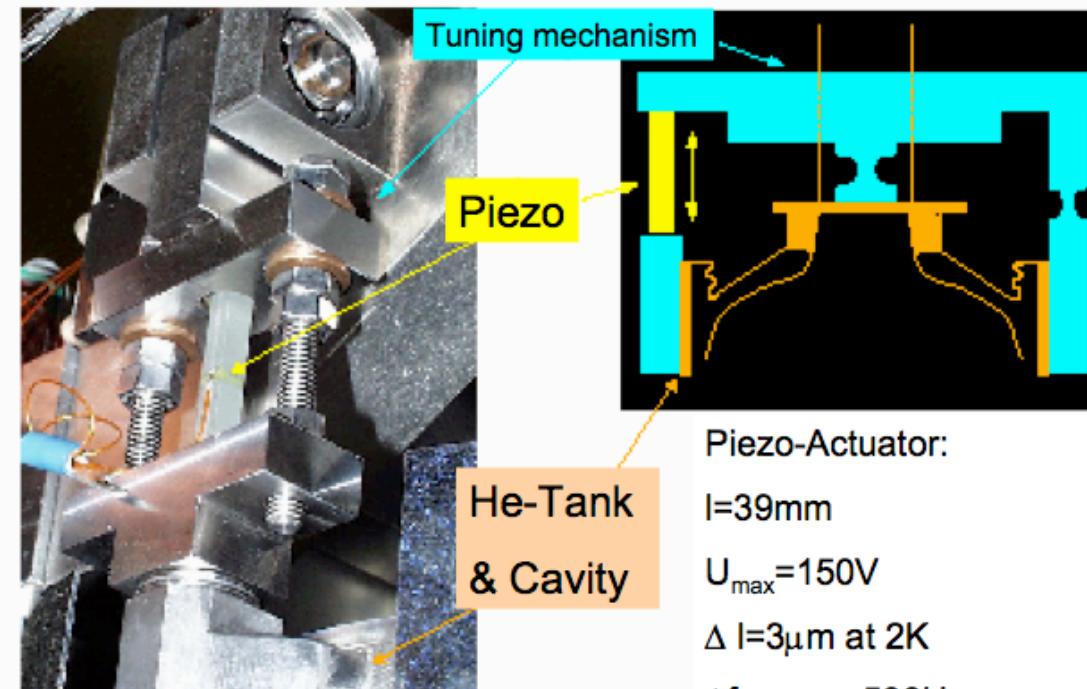


Lutz Lilje DESY

TESLA

26/01/2004

Ralph J. Pasquinelli

Piezo Tuner Response


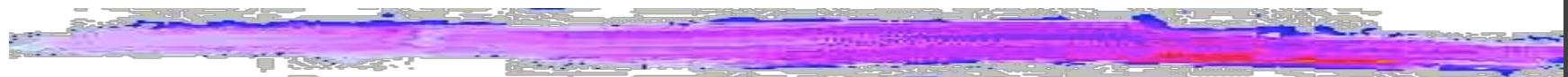


Frequency stabilization
during RF pulse using a
piezoelectric tuner

Blue: With piezo

Red: Without piezo

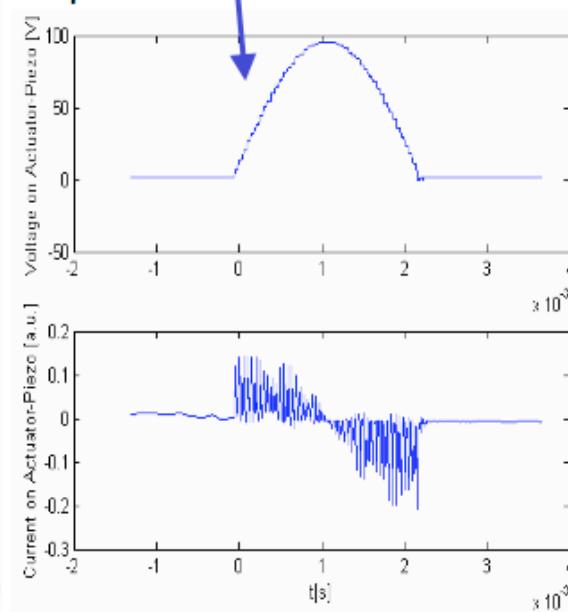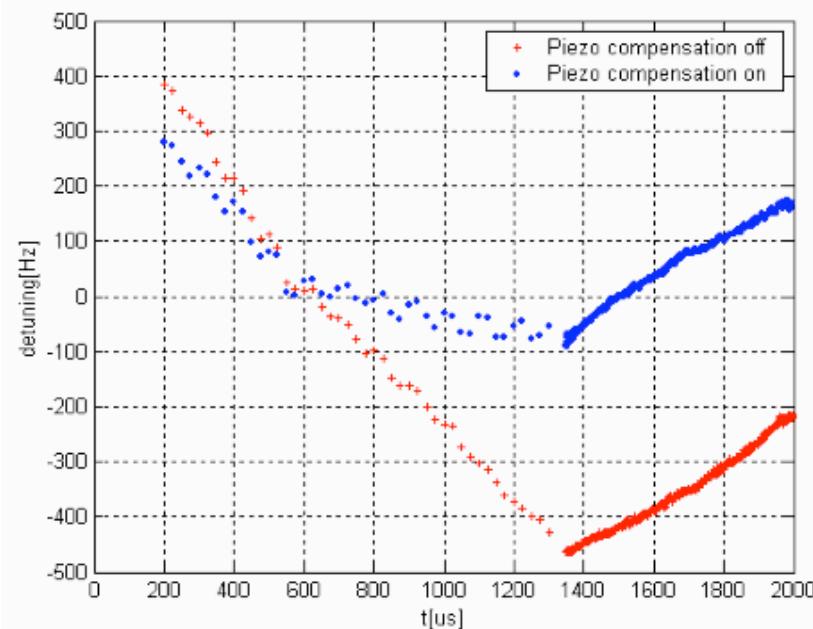Frequency detuning of 500 Hz compensated
voltage pulse (~100 V) on the piezo. No
resonant compensation



Lutz Lilje DESY

TESLA


26/01/2004

Ralph J. Pasquinelli

Cavity Amplitude and Phase Response



RF signals at 35 MV/m

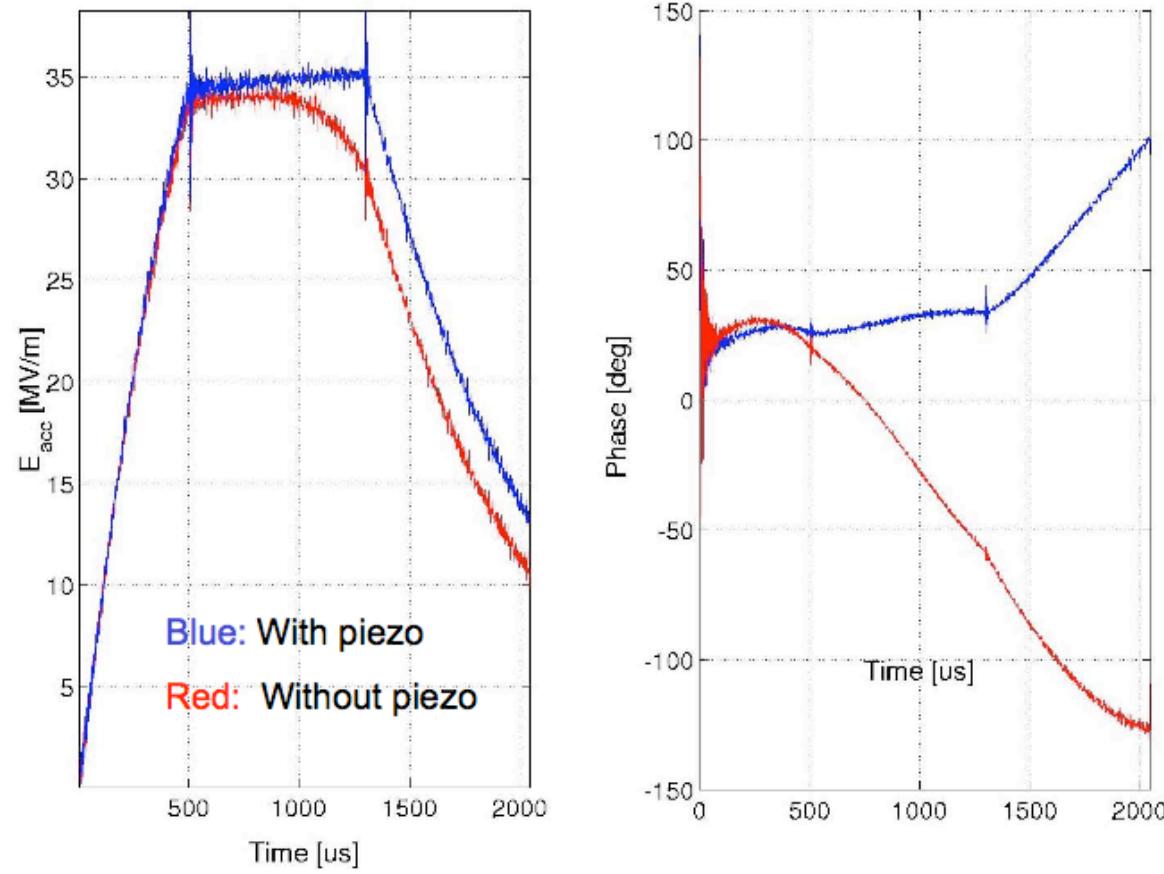

Lutz Lilje
DESY

Ralph J. Pasquinelli

Sources of Microphonic Noise



Cultural Noise






Earthquakes



Vacuum Pumps

Ralph J. Pasquinelli

Microphonics Compensation

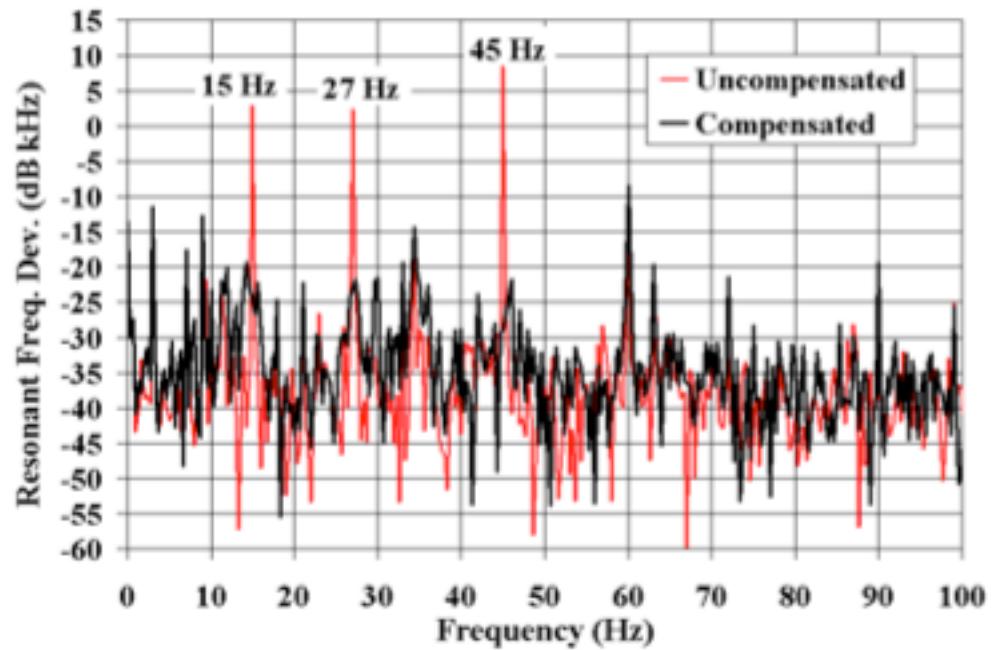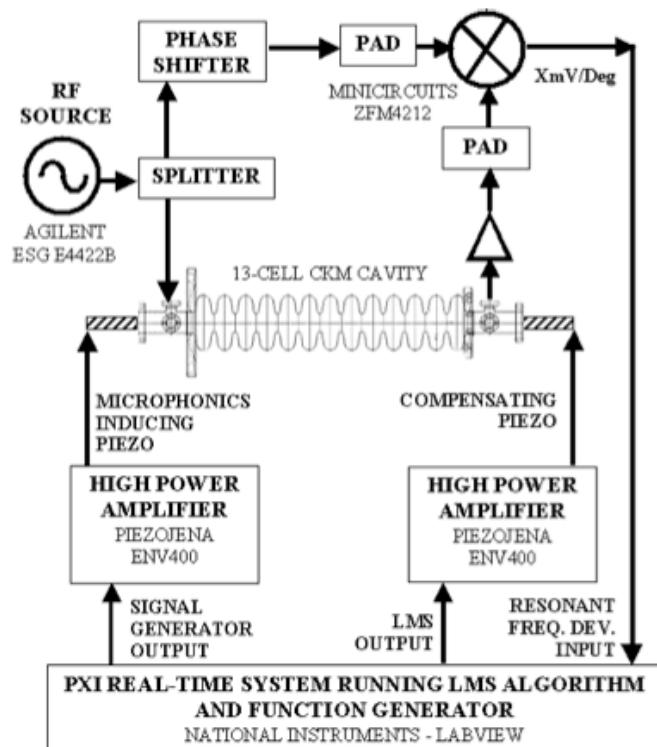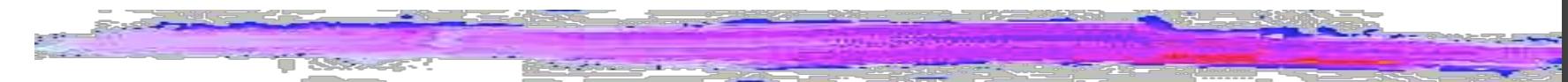


Ruben Carcagno et al Fermilab

Ralph J. Pasquinelli

Beam impedance loads SRF cavity



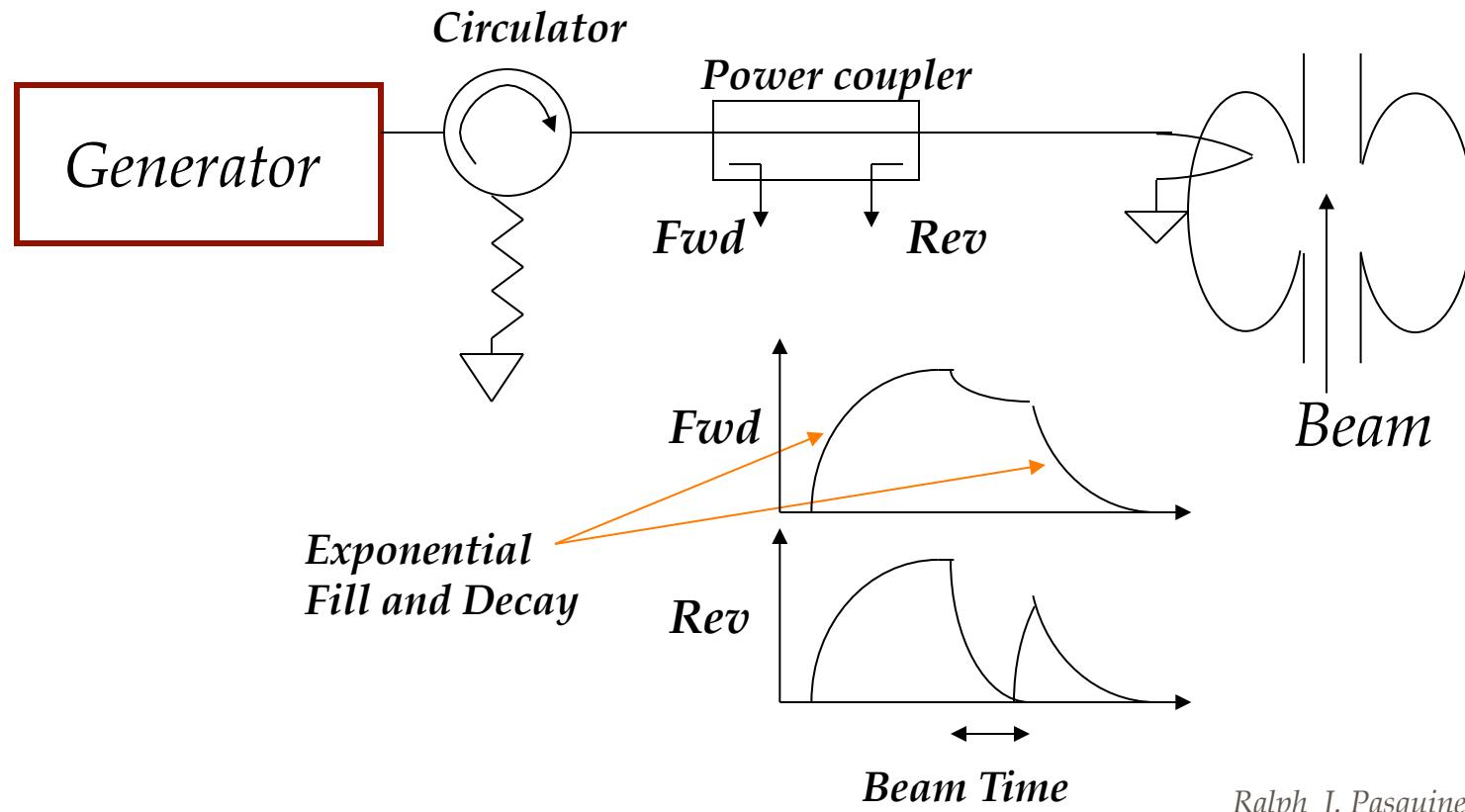Drive to cavity is only matched when beam is present




Ralph J. Pasquinelli

Low Level RF (LLRF)




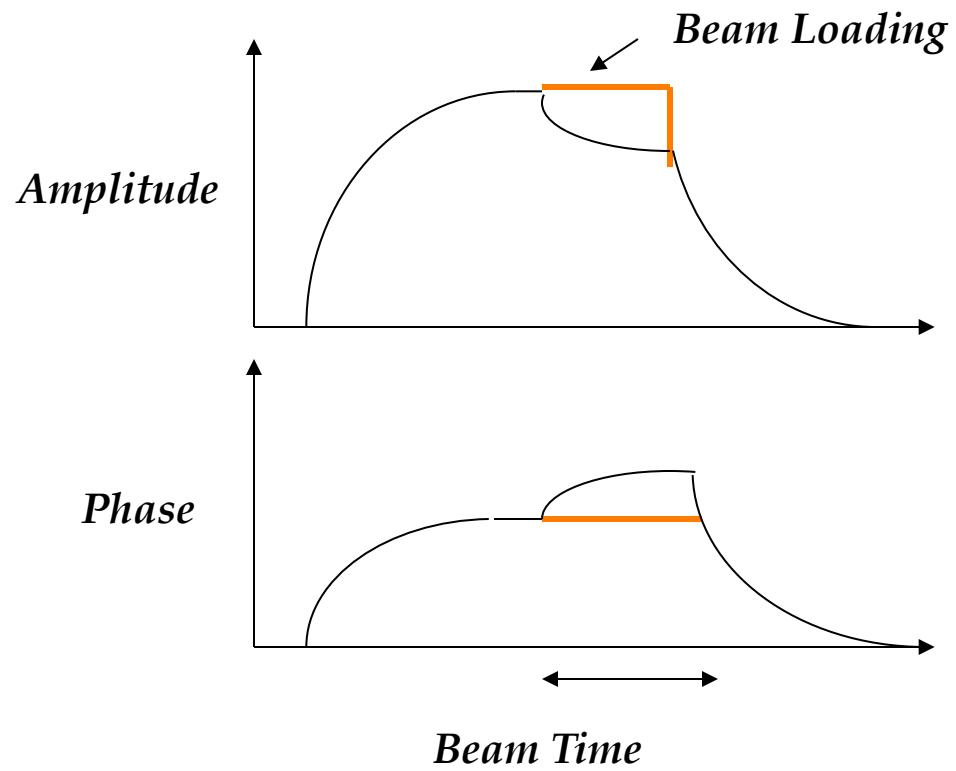Provides feedback and feed forward to improve gradient stability



Ralph J. Pasquinelli

Typical LLRF Hardware

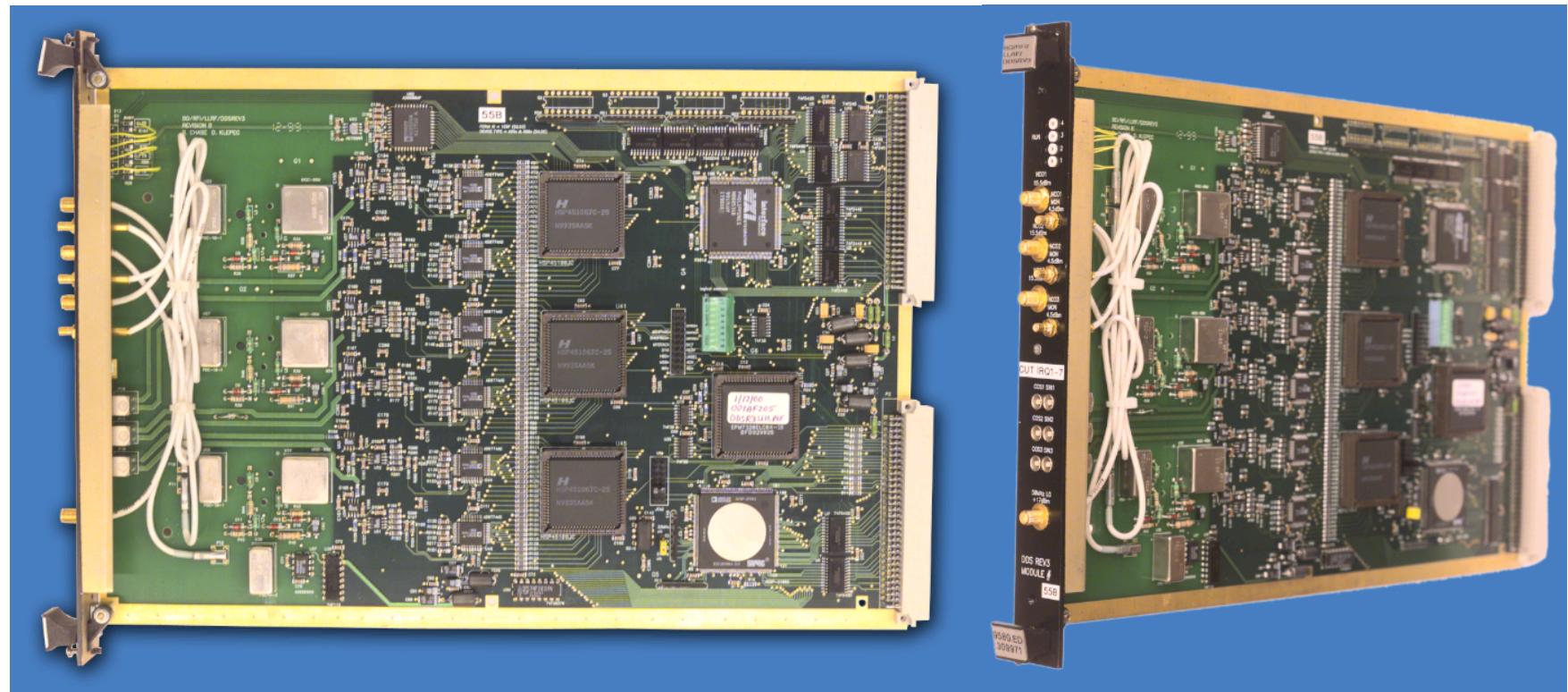



Ralph J. Pasquinelli

Main Injector, Recycler, and Tevatron LLRF at Fermilab



Ralph J. Pasquinelli

Cavity Higher Order Modes (HOMs)

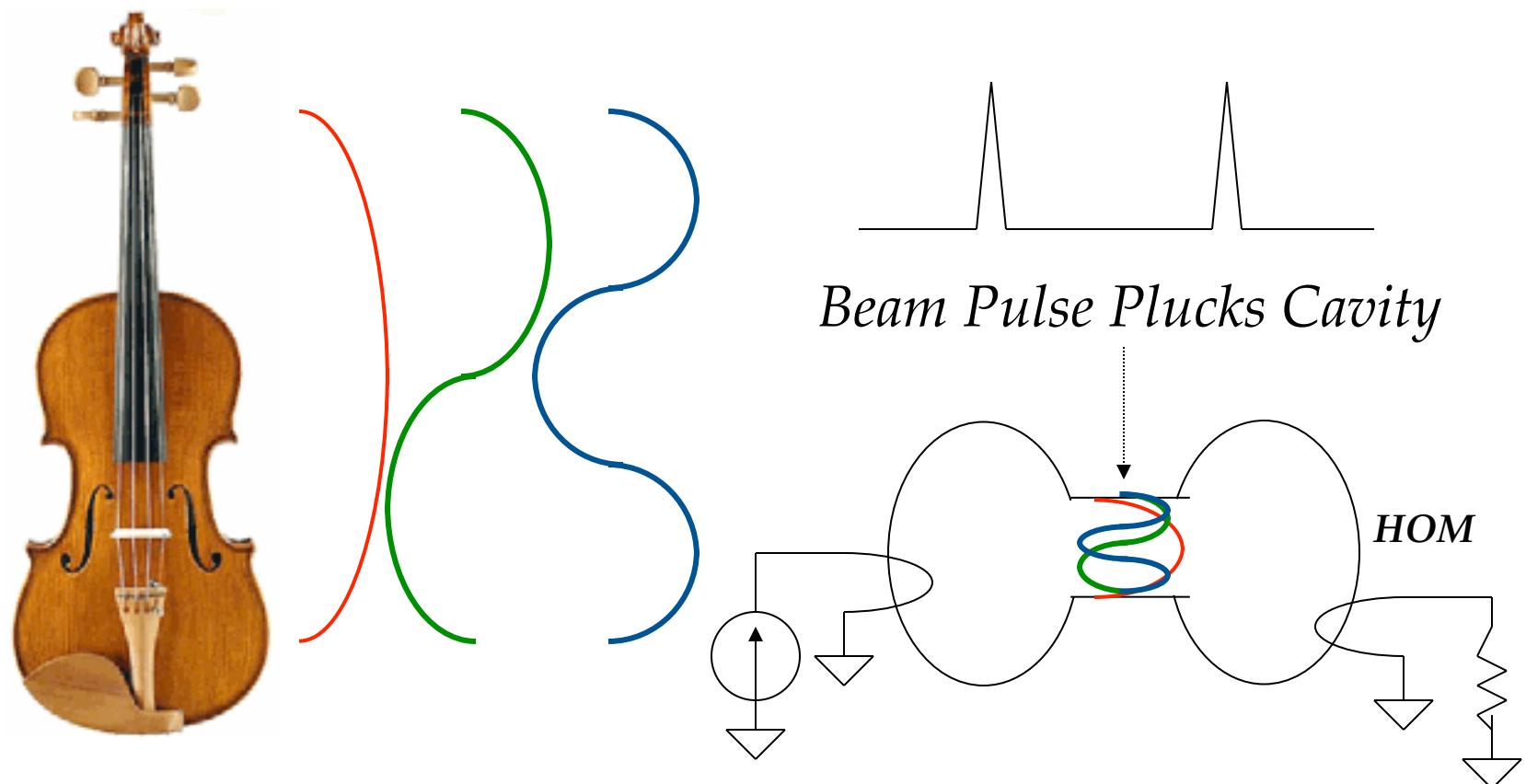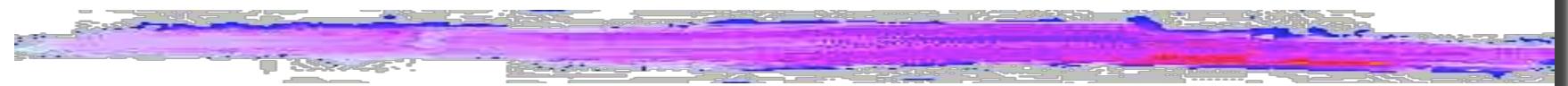


Beam Pulse Plucks Cavity

Ralph J. Pasquinelli

More choices....




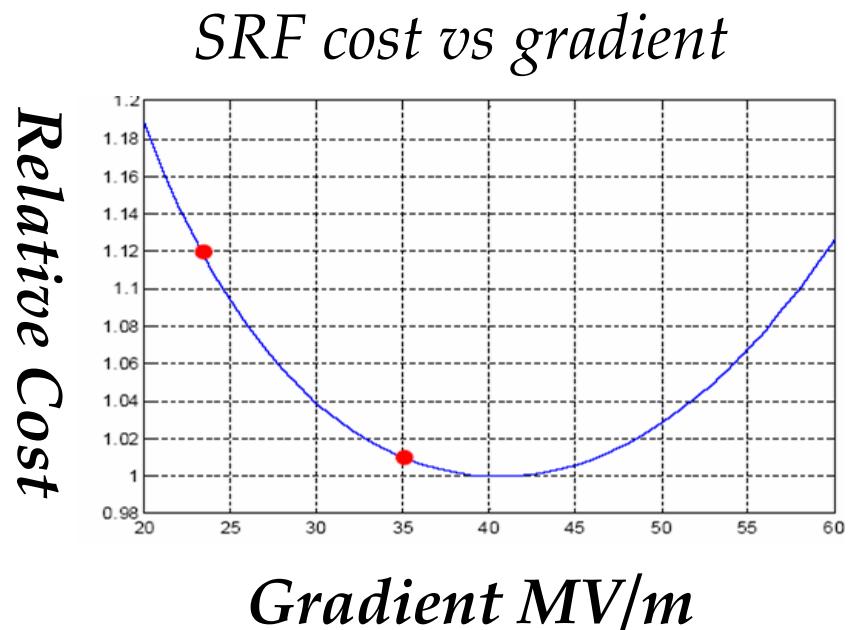
- Energy of the accelerator?*
- Gradient of cavities?*
- Duty cycle and repetition rate?*
- Location of hardware?*



C. Adolphsen (SLAC)


Ralph J. Pasquinelli

Tunnel Topology Options

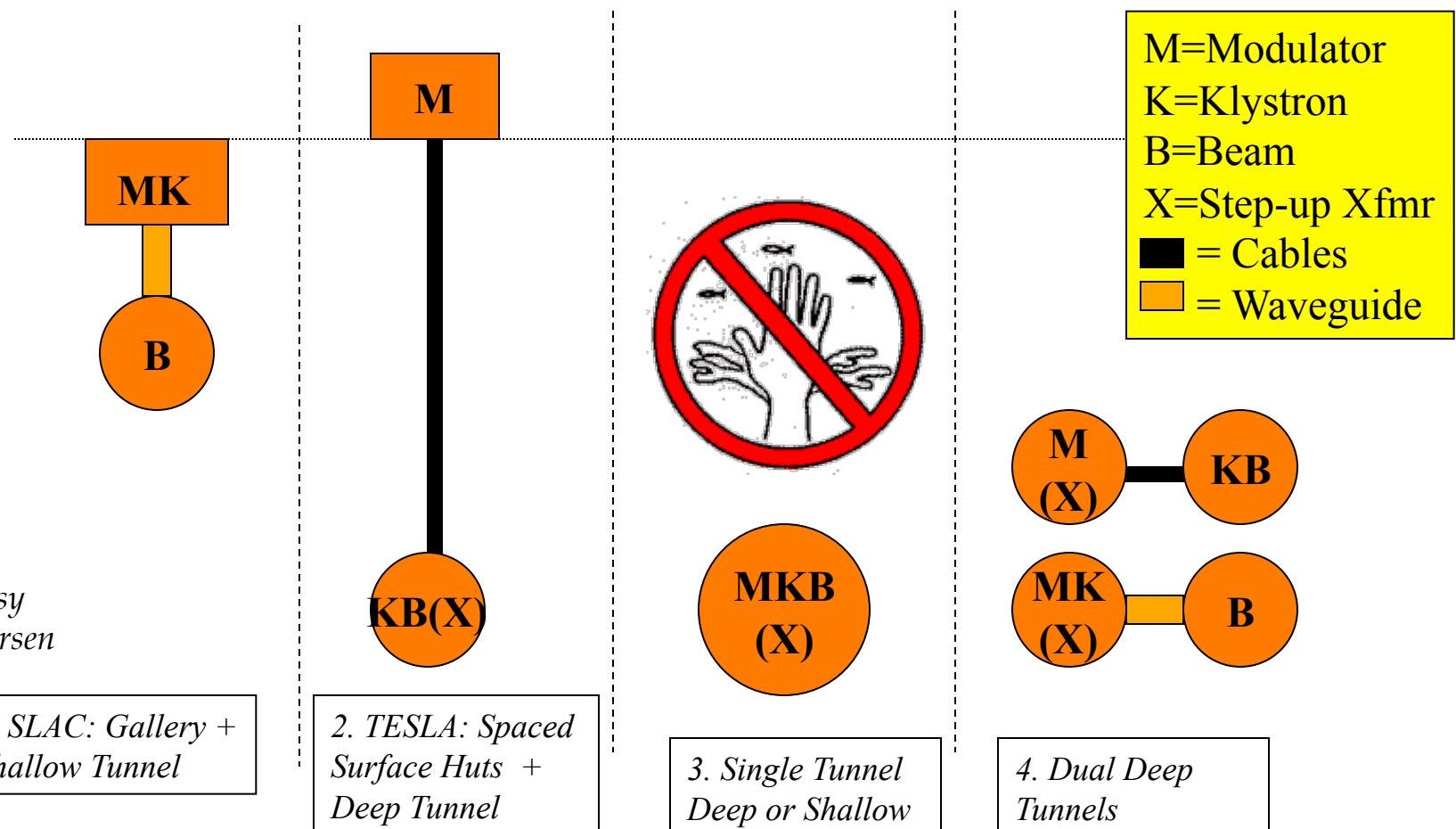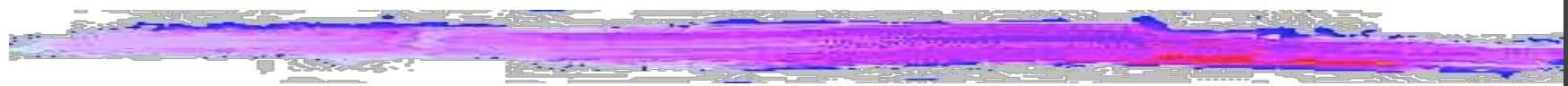

Ralph J. Pasquinelli


Typical RF Station

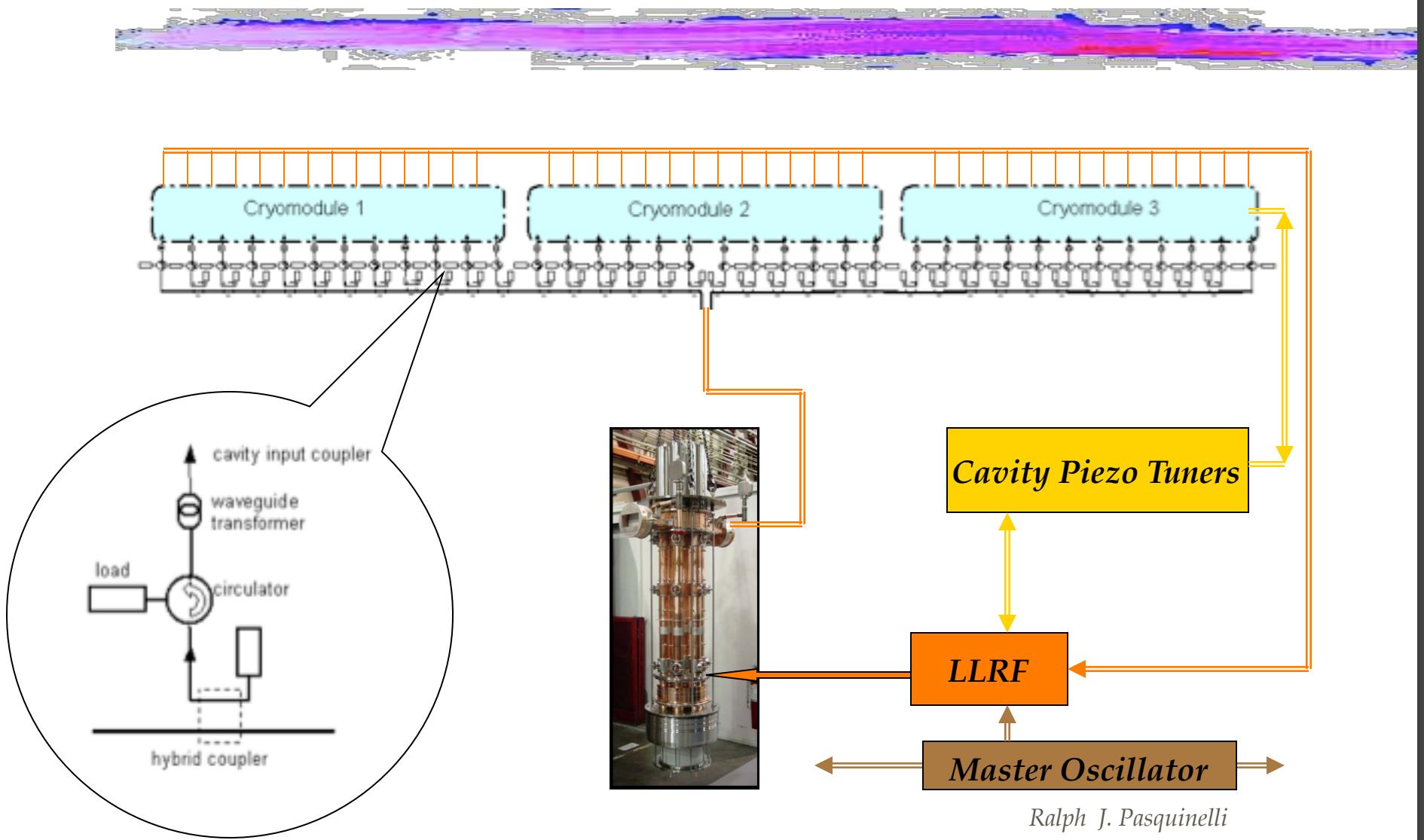

Crab Cavities



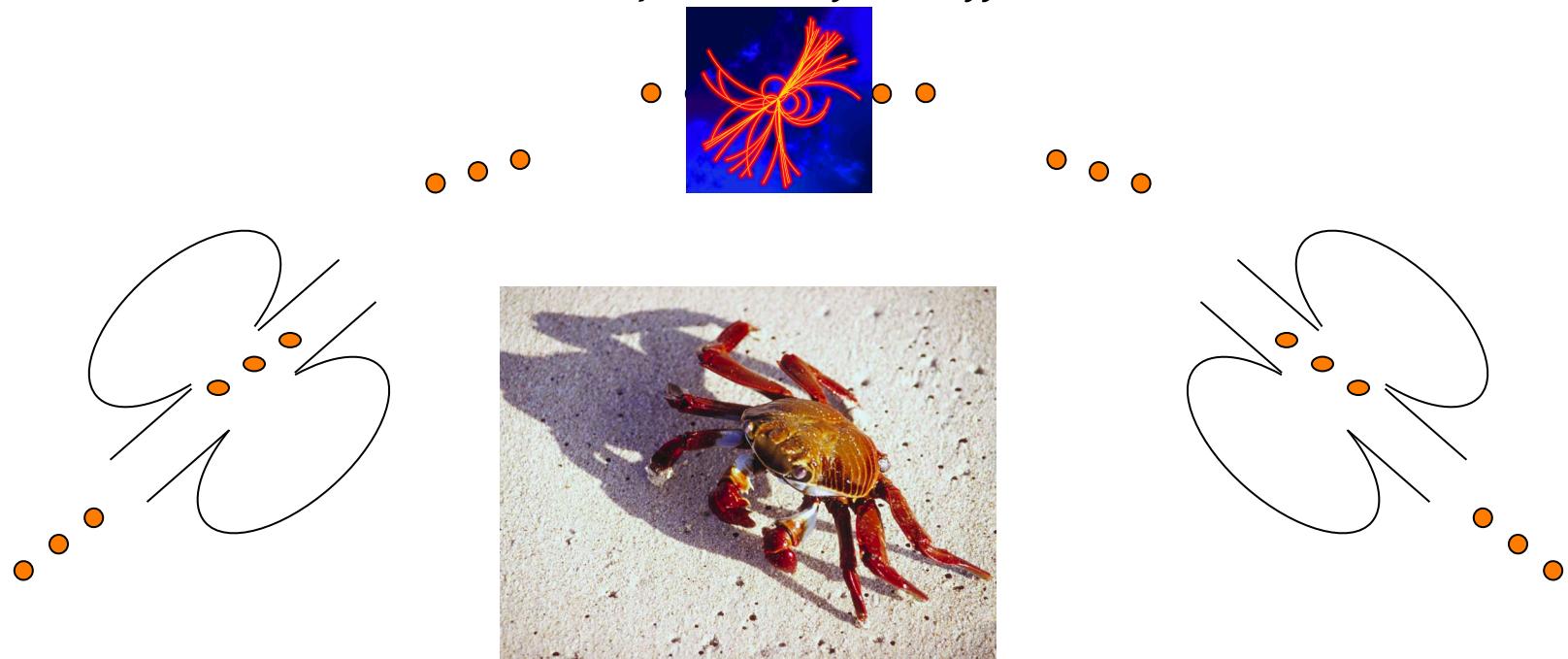RF Used to Compensate for Off Axis Collisions



Ralph J. Pasquinelli

Overall RF Power Conversion Efficiency



37%-48%


RF Power Source



AC to DC Power Converter



Transmission Line

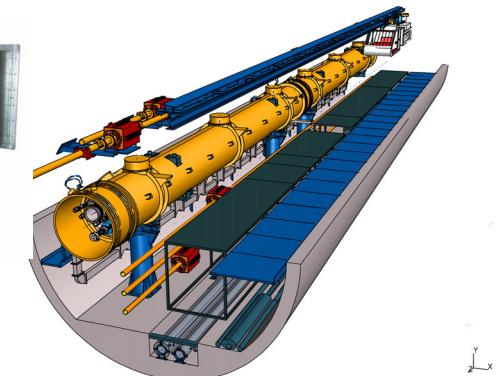

Wall Plug

78%

50%-65%

95%

Beam

Ralph J. Pasquinelli

Cost of RF Power



*RF Power Source
AC to DC conversion
LLRF & Interocks
Power distribution
+ Controls*

\$0.25 to \$15 per RF Watt

Ralph J. Pasquinelli

This Concludes Microwave Measurements 101 Lectures!



Ralph J. Pasquinelli